

Electricity

NCERT Class 10 Science Chapter 11 (Hinglish Detailed Notes)
NCERT Class 10 Science Ch-11 | Hinglish Detailed Notes

COLOUR CODE: RED = Core Basics / extra help (Class 7-8-9 wali cheezein jo yaad honi chahiye).

COLOUR CODE: GREEN = Board exam me ye topics BAAR-BAAR aate hain - pakka yaad karo.

Baaki normal black text = main chapter content (detail me, simple bhasha me).

CORE BASICS - PEHLE YE PADHO (CLASS 7-8-9 KA FOUNDATION)

Tune 7-8-9 nahi padhi - koi tension nahi. Ye page is chapter ki base hai.

Numerical-heavy chapter hai, isliye base + formula rearrange karna pakka aana chahiye.

1) ELECTRIC CHARGE kya hai?

- Har cheez atom se bani; atom me electron (-ve) aur proton (+ve) hote.
- ELECTRON ke paas chhota -ve charge hota. Charge ka SI unit = COULOMB (C).
- 1 electron ka charge = 1.6×10^{-19} C (yaani 1 C me $\sim 6.25 \times 10^{18}$ electron).
- Charge ka behna (flow) hi CURRENT kehlata hai.

2) CONDUCTOR vs INSULATOR:

- CONDUCTOR = current paas hone de (metal: Cu, Al; free electron hote).
- INSULATOR = current na de (rubber, plastic, wood, glass).

3) CELL aur BATTERY:

- CELL = ek device jo chemical energy ko electric energy me badle; do terminal hote - bada/lamba = +ve, chhota = -ve.
- BATTERY = do ya zyada cell ka combination (zyada voltage ke liye).

4) CIRCUIT kya hai?

- CIRCUIT = ek BAND (closed) raasta jisme current ghoom ke wapas aaye.
- Switch ON = circuit closed (current chale); switch OFF = open (na chale).

5) COMMON CIRCUIT SYMBOLS (yaad rakho - diagram me kaam aayenge):

- Cell → ek lamba patli line (+) aur ek chhoti moti line (-).
- Battery → do ya zyada cell side by side.
- Bulb → circle ke andar cross (X) ya loop (filament).
- Switch/Key → ek gap with ek chhoti line (open/close).
- Wire/Conductor → seedhi line.
- Resistor → ek rectangle (box) ya zig-zag line.
- Ammeter → circle ke andar letter A.
- Voltmeter → circle ke andar letter V.

6) CURRENT aur VOLTAGE simple words me:

- CURRENT (I) = wire me charge kitni tezi se beh raha (paani ke flow jaisa).
- VOLTAGE/POTENTIAL DIFFERENCE (V) = charge ko dhakelne wala "push" (paani ke pipe me pressure jaisa). Cell ye push deti hai.

7) SERIES vs PARALLEL (intro):

- SERIES = sab components ek hi line/raaste me ek ke baad ek jude.
- PARALLEL = components alag-alag branch me jude (ek hi do point ke beech).

8) UNITS TABLE (is chapter ke main units):

- Current (I) → AMPERE (A)
- Charge (Q) → COULOMB (C)
- Potential diff (V) → VOLT (V)
- Resistance (R) → OHM (ohm)
- Resistivity (rho) → ohm*m (ohm metre)
- Power (P) → WATT (W)

- Energy -> JOULE (J) ya kWh (kilowatt-hour)

9) FORMULA REARRANGE karna (basic algebra - bahut zaroori):

- Agar $V = I R$ hai to: $I = V / R$ aur $R = V / I$.
- Yaani jis cheez ko nikalna ho, use akela karo, baaki cheezein dusri taraf.
- Triangle trick: V upar, (I R) niche -> ungli se dhako jo chahiye.
- Units bhi saath le ke chalo (V = volt, A = ampere, ohm = ohm).

1. ELECTRIC CURRENT (VIDYUT DHARA)

DEFINITION: Electric current = kisi conductor ke cross-section se per second behne wale charge ki maatra. Yaani current = charge / time.

FORMULA: $I = Q / t$

- I = current (ampere, A), Q = charge (coulomb, C), t = time (second, s).
- Isse: $Q = I \times t$ aur $t = Q / I$.

UNIT: AMPERE (A). $1 \text{ A} = 1 \text{ C} / \text{s}$

- Matlab agar 1 second me 1 coulomb charge beh raha to current = 1 ampere.
- Chhoti current ke liye: 1 mA (milliampere) = 10^{-3} A ,
 $1 \text{ microampere} = 10^{-6} \text{ A}$.

CURRENT KI DIRECTION (exam favourite):

- CONVENTIONAL current ki direction = +ve charge ke behne ki direction (yaani +ve terminal se -ve terminal taraf bahar circuit me).
- ELECTRON asal me -ve terminal se +ve terminal jaate (ulti direction).
- To conventional current, electron flow ke ULT (opposite) maana jaata.

MAAPNA (measure): current AMMETER se naapte.

- Ammeter ko hamesha SERIES me jodte (jis component me current naapni ho).
- Ideal ammeter ka resistance ZERO (taaki current par asar na pade).

2. ELECTRIC POTENTIAL & POTENTIAL DIFFERENCE

POTENTIAL DIFFERENCE (V) = do point ke beech unit charge ko le jaane me kiya gaya KAAM (work). Yahi charge ko circuit me dhakelta hai.

FORMULA: $V = W / Q$

- V = potential difference (volt, V), W = work/energy (joule, J),
Q = charge (coulomb, C).
- Isse: $W = V \times Q$ aur $Q = W / V$.

UNIT: VOLT (V). $1 \text{ V} = 1 \text{ J} / \text{C}$

- Matlab 1 coulomb charge ko le jaane me 1 joule kaam lage to $V = 1 \text{ volt}$.

MAAPNA (measure): potential difference VOLTMETER se naapte.

- Voltmeter ko hamesha PARALLEL me jodte (jin do point ke beech V naapni ho).
- Ideal voltmeter ka resistance INFINITE (bahut bada) hota.

Yaad rakhne ki trick:

- Ammeter -> A -> "A" se "series" (current naapta, series me).
- Voltmeter -> Parallel me (potential difference naapta).

3. CIRCUIT DIAGRAM & SYMBOLS

- Circuit diagram = circuit ko symbols se draw karna (asli device ke bajaye).
- Faayda: samajhna aur banana aasaan, sabhi same symbol use karte.

COMMON SYMBOLS (revision):

- Cell / Battery, Bulb, Switch (key), Wire, Resistor (box/zig-zag),
Ammeter (A in circle, series), Voltmeter (V in circle, parallel),
Variable resistor / Rheostat (resistor with arrow).
- Ek simple circuit: Cell -> switch -> bulb/resistor -> wapas cell.
Ammeter series me, voltmeter resistor ke parallel me.

4. OHM'S LAW (BAHUT IMPORTANT)

OHM'S LAW: Constant temperature par, ek conductor me behne wali current (I) uske beech ke potential difference (V) ke DIRECTLY PROPORTIONAL hoti hai.

V proportional to I $\Rightarrow V = I R$

FORMULA: $V = I R$

- V = potential difference (V), I = current (A), R = resistance (ohm).

- Isse: $I = V / R$ aur $R = V / I$.

V-I GRAPH:

- V ko y-axis, I ko x-axis par lo $\rightarrow$ graph ek SEEDHI LINE (straight line)

origin se hoti hui aati hai.

- Line ka SLOPE = $V / I = R$ (resistance). Zyada slope $\rightarrow$ zyada resistance.

RESISTANCE (R):

- $R = V / I$. Ye conductor ka current ke flow ke against "rukaawat" (opposition).

- UNIT: OHM (likhte: ohm). 1 ohm = 1 volt / 1 ampere.

- 1 ohm = jab 1 V lagane par 1 A current behti.

Note: jo conductor Ohm's law follow kare = OHMIC (e.g. metal wire).

Jo na follow kare (graph straight line na ho) = NON-OHMIC (e.g. bulb, diode).

5. RESISTANCE & FACTORS (RESISTIVITY)

Conductor ka resistance (R) in cheezon par depend karta hai:

- (i) LENGTH (L): R, length ke DIRECTLY proportional. Lamba taar -> zyada R.
- (ii) AREA (A): R, cross-section area ke INVERSELY proportional.
Mota taar (zyada area) -> kam R.
- (iii) MATERIAL: har material ka apna RESISTIVITY (ρ) hota.
- (iv) TEMPERATURE: temperature badhne par (metal me) R badh jaata.

FORMULA: $R = \rho * L / A$

- ρ (ρ) = resistivity, L = length (m), A = area (m^2).
- Isse: $\rho = R * A / L$.

RESISTIVITY (ρ):

- DEFINITION: ρ = us material ke 1 m lambe aur 1 m^2 area wale tukde ka resistance. Ye material ki apni property hai (size par depend nahi karti).
- UNIT: $ohm * m$ (ohm metre).

CONDUCTOR vs INSULATOR by resistivity:

- CONDUCTOR (metal): bahut KAM resistivity ($10^{-8} ohm * m$ range).
- INSULATOR (rubber, glass): bahut ZYADA resistivity ($10^{12} ohm * m$ range).
- ALLOY (nichrome, manganin): conductor se zyada resistivity + heat me jaldi oxidise nahi hote -> isiliye heating elements me use hote.

Note: silver sabse achha conductor (sabse kam resistivity), uske baad copper.
Ghar ki wiring me COPPER / ALUMINIUM use hota (kam resistivity, saste).

6. RESISTORS IN SERIES

SERIES me resistors ek ke baad ek (single line) jude hote.

KEY POINTS:

- Har resistor me SAME current (I) behti.
- Total voltage = har resistor ke voltage ka JOD (sum):
 $V = V_1 + V_2 + V_3$.
- EQUIVALENT (total) RESISTANCE: $R_s = R_1 + R_2 + R_3$
- Series me total resistance hamesha sabse BADE resistor se bhi ZYADA hoti.

Drawback: ek component fuse/kharab ho to poora circuit band (purani jhaalar ki tarah - ek bulb gaya to sab band). Isliye ghar me series use nahi karte.

7. RESISTORS IN PARALLEL

PARALLEL me sab resistors ek hi do point ke beech alag-alag branch me jude.

KEY POINTS:

- Har resistor par SAME voltage (V) lagta.
- Total current = har branch ki current ka JOD: $I = I_1 + I_2 + I_3$.
- EQUIVALENT RESISTANCE: $1 / R_p = 1/R_1 + 1/R_2 + 1/R_3$
- Parallel me total resistance hamesha sabse CHHOTE resistor se bhi KAM hoti.

GHAR KE APPLIANCES PARALLEL ME KYUN? (exam me pakka aata)

- Har appliance ko same full voltage (220 V) milta.
- Ek band ho to baaki chalte rehte (independent on/off).
- Har device apni zaroorat ki current le sakta (total R kam -> zyada current).

8. HEATING EFFECT OF CURRENT (JOULE'S LAW)

Jab current resistor se behti to resistance ki wajah se HEAT paida hoti - isko current ka HEATING EFFECT kehte.

JOULE'S LAW OF HEATING: $H = I^2 \cdot R \cdot t$

- H = heat (joule, J), I = current (A), R = resistance (ohm), t = time (s).
- Heat directly proportional to: I ke square, R , aur time t .

Why heat? Current behne wale electron, conductor ke ions se takraate, jisse energy heat ke roop me release hoti.

APPLICATIONS (heating effect ka use):

- ELECTRIC HEATER / IRON / TOASTER / GEYSER: nichrome alloy ka coil (high resistivity + high melting point) garam ho jaata.
- ELECTRIC BULB: tungsten FILAMENT (bahut high melting point ~ 3380 C) garam ho ke chamakta (roshni deta).
- ELECTRIC FUSE (safety device): niche detail me.

ELECTRIC FUSE (bahut important):

- Ek patla taar (tin + lead alloy) jiska melting point KAM hota.
- Circuit ke SERIES me lagaya jaata.
- Jab current safe limit se zyada ho jaye (short circuit / overload), fuse wire $H = I^2 R t$ se garam ho ke PIGHAL jaata $\rightarrow$ circuit TOOT jaata.
- Isse appliance aur aag se bachaav hota. Yahi fuse ka kaam hai.

9. ELECTRIC POWER (VIDYUT SHAKTI)

ELECTRIC POWER (P) = per second me use/kharch hone wali electric energy (rate).

FORMULAE (teeno yaad rakho):

$$P = V I \quad (\text{power} = \text{voltage} \times \text{current})$$

$$P = I^2 \times R \quad (V = IR \text{ daal ke})$$

$$P = V^2 / R \quad (I = V/R \text{ daal ke})$$

- P = power (watt, W), V = volt, I = ampere, R = ohm.

UNIT: WATT (W). $1 \text{ W} = 1 \text{ V} \times 1 \text{ A} = 1 \text{ J/s}$.

- Bada unit: 1 kilowatt (kW) = 1000 W.

ELECTRIC ENERGY: $E = P \times t$ (power x time).

- SI unit = JOULE (J). Par bijli ka bill JOULE me nahi, bada unit chahiye.

COMMERCIAL UNIT OF ENERGY = KILOWATT-HOUR (kWh) - "1 UNIT" of electricity.

- 1 kWh = 1 kW ka appliance 1 ghante (hour) chalane par use hui energy.

- CONVERSION: $1 \text{ kWh} = 1000 \text{ W} \times 3600 \text{ s} = 3.6 \times 10^6 \text{ J}$.

ELECTRICITY BILL - UNITS KAISE NIKALE:

- Units (kWh) = Power(kW) x time(hours used).

- Total units x rate-per-unit = bill amount.

- Tip: Watt ko 1000 se divide karke kW banao; minutes ko 60 se divide karke hours banao.

10. SOLVED EXAMPLES (HARDEST -> EASIEST)

Ye type ke numericals exam me pakka aate - steps + UNITS khud likhke practice karo.

EXAMPLE 1 (Hardest): Combination - 6 ohm aur 3 ohm PARALLEL me hain, aur ye combination 4 ohm ke saath SERIES me. Source = 12 V. Equivalent R aur total current nikaalo.

Step 1 - Parallel part (6 aur 3):

$$1/R_p = 1/6 + 1/3 = 1/6 + 2/6 = 3/6 = 1/2 \rightarrow R_p = 2 \text{ ohm.}$$

Step 2 - Ab R_p (2 ohm) series me 4 ohm ke saath:

$$R(\text{total}) = 2 + 4 = 6 \text{ ohm.}$$

Step 3 - Total current (Ohm's law):

$$I = V / R = 12 / 6 = 2 \text{ A.}$$

ANSWER: Equivalent R = 6 ohm, total current = 2 A.

EXAMPLE 2: Parallel - 4 ohm aur 6 ohm parallel me 12 V se jude. R_p aur har branch ki current nikaalo.

Step 1 - Equivalent:

$$1/R_p = 1/4 + 1/6 = 3/12 + 2/12 = 5/12 \rightarrow R_p = 12/5 = 2.4 \text{ ohm.}$$

Step 2 - Parallel me har branch par same V = 12 V:

$$I_1 = V/R_1 = 12/4 = 3 \text{ A}$$

$$I_2 = V/R_2 = 12/6 = 2 \text{ A}$$

Step 3 - Check total: $I = I_1 + I_2 = 3 + 2 = 5 \text{ A}$ (= $12/2.4$, sahi).

ANSWER: $R_p = 2.4 \text{ ohm}$, $I_1 = 3 \text{ A}$, $I_2 = 2 \text{ A}$.

EXAMPLE 3: Power & bill - ek 1000 W (1 kW) heater roz 2 ghante, 30 din chalta.

Rate = Rs 5 per unit. Mahine ka bill nikaalo.

Step 1 - Power = 1000 W = 1 kW.

Step 2 - Time = 2 h/day x 30 = 60 hours.

Step 3 - Energy = $P \times t = 1 \text{ kW} \times 60 \text{ h} = 60 \text{ kWh}$ (= 60 units).

Step 4 - Bill = $60 \times 5 = \text{Rs } 300$.

ANSWER: 60 units, bill = Rs 300.

EXAMPLE 4: Joule heating - ek 5 ohm resistor me 2 A current 5 minute behti.

Kitni heat (H) paida hui?

Step 1 - t ko second me: 5 min = $5 \times 60 = 300 \text{ s}$.

Step 2 - $H = I^2 \times R \times t = (2)^2 \times 5 \times 300 = 4 \times 5 \times 300 = 6000 \text{ J}$.

ANSWER: $H = 6000 \text{ J}$ (= 6 kJ).

EXAMPLE 5: Ohm's law - ek bulb par 220 V lagne par 0.5 A current behti.

Resistance nikaalo.

$$R = V / I = 220 / 0.5 = 440 \text{ ohm.}$$

ANSWER: $R = 440 \text{ ohm}$.

EXAMPLE 6: $R = \rho \cdot L/A$ - agar ek taar ki LENGTH double kar di jaye (area same), to resistance par kya asar? Aur agar AREA double ho (length same) to?

- R proportional to L: length double -> R bhi DOUBLE (2 guna).

- R proportional to $1/A$: area double -> R HALF (aadha) ho jaata.

ANSWER: length double => $R \times 2$; area double => $R / 2$.

EXAMPLE 7 (Easiest): $I = Q/t$ - ek conductor se 60 C charge 2 minute me behta.

Current nikaalo.

Step 1 - $t = 2 \text{ min} = 120 \text{ s}$.

Step 2 - $I = Q / t = 60 / 120 = 0.5 \text{ A}$.

ANSWER: $I = 0.5 \text{ A}$.

11. QUICK Q&A - PADHNE KE BAAD KHUD CHECK KARO

Pehle khud answer socho, fir niche milao. Ye board-style questions hain.

Q1. Electric current kya hai aur uska SI unit?

A1. Per second behne wala charge; $I = Q/t$. SI unit = ampere (A), $1 \text{ A} = 1 \text{ C/s}$.

Q2. Ammeter aur Voltmeter circuit me kaise jodte hain?

A2. Ammeter SERIES me (current naapne), Voltmeter PARALLEL me (potential difference naapne). Ideal ammeter $R = 0$, ideal voltmeter $R = \text{infinite}$.

Q3. Ohm's law likho aur V-I graph kaisa hota?

A3. Constant temp par V proportional to I, yaani $V = IR$. V-I graph origin se nikalti SEEDHI LINE; slope = R.

Q4. Resistance kin cheezon par depend karta? Formula?

A4. Length (proportional L), area (proportional $1/A$), material (ρ), temperature.
 $R = \rho \cdot L/A$. Resistivity ka unit = $\text{ohm} \cdot \text{m}$.

Q5. Series me equivalent resistance aur ek nuksan?

A5. $R_s = R_1 + R_2 + R_3$. Nuksan: ek component kharab to poora circuit band.

Q6. Parallel ka formula aur ghar me parallel kyun?

A6. $1/R_p = 1/R_1 + 1/R_2 + \dots$. Ghar me: har appliance ko full voltage milta aur ek band ho to baaki chalte.

Q7. Joule's law of heating likho aur ek application.

A7. $H = I^2 \cdot R \cdot t$. Application: electric heater/iron/bulb filament/fuse.

Q8. Electric fuse kaise kaam karta?

A8. Kam melting point ka patla taar series me; zyada current par $H = I^2 R t$ se pighal ke circuit tod deta (overload/short circuit se bachaav).

Q9. Electric power ke teeno formula aur unit?

A9. $P = VI = I^2 R = V^2 / R$. Unit = watt (W); $1 \text{ W} = 1 \text{ J/s}$.

Q10. 1 unit bijli = kitna? (kWh aur joule me)

A10. $1 \text{ unit} = 1 \text{ kWh} = 1000 \text{ W} \times 3600 \text{ s} = 3.6 \times 10^6 \text{ J}$.

EXAM STRATEGY (1 minute revision):

- Ohm's law $V = IR$ + V-I straight line graph (slope = R) - pakka aata.
 - $R = \rho \cdot L/A$ + 4 factors (length, area, material, temperature).
 - Series $R_s = R_1 + R_2 + R_3$; Parallel $1/R_p = 1/R_1 + 1/R_2 + \dots$ (signs/steps yaad).
 - Joule's law $H = I^2 R t$ + fuse working - scoring topic.
 - Power $P = VI = I^2 R = V^2/R$ aur $1 \text{ kWh} = 3.6 \times 10^6 \text{ J}$ + bill nikaalna.
 - Numericals me UNITS likhna mat bhoolo (marks katte hain warna).
 - CORE BASICS page (charge, circuit, symbols, formula rearrange) bhool jaao to wapas pehle padho - base strong rakho.
-

